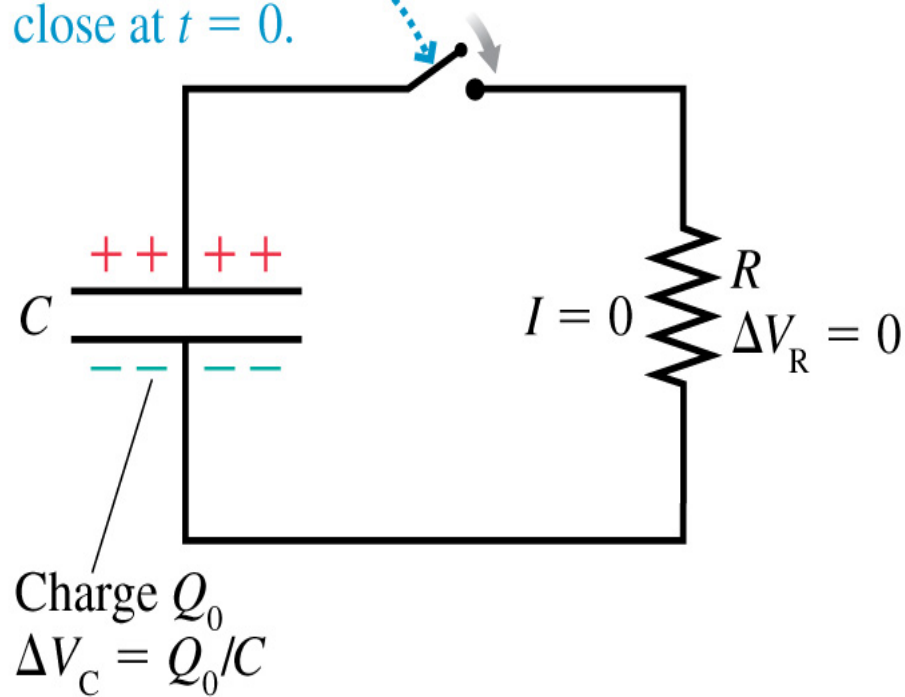


Lecture 13: Chapter 32, RC-circuit, October 18 2005


(a) Before the switch closes

The switch will
close at $t = 0$.



The capacitor is charged

(b) After the switch closes

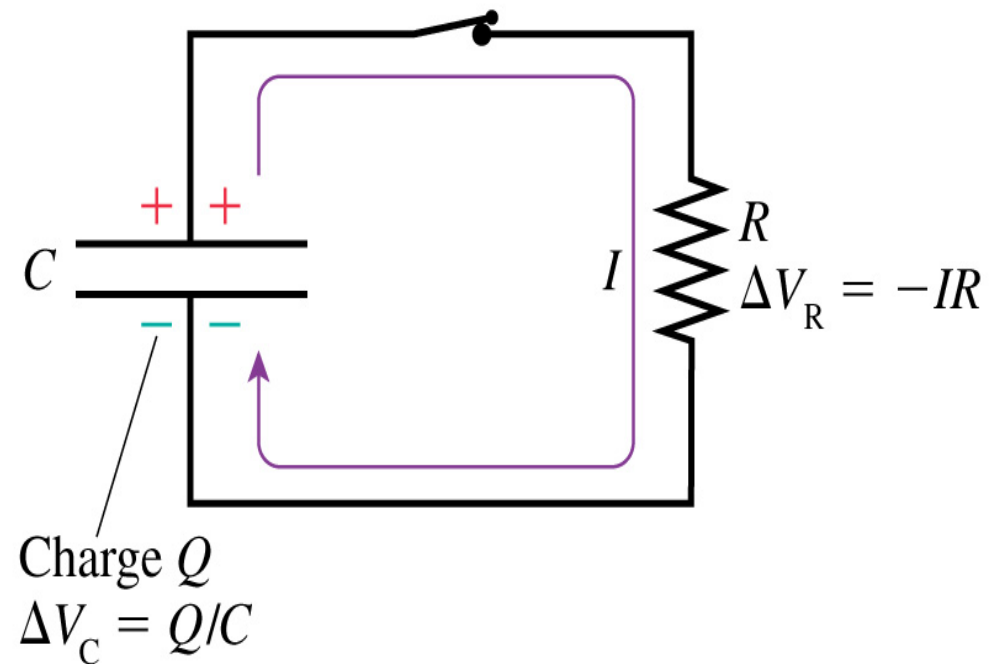



The capacitor is discharging

RC-circuit

Note Title

3/22/2005

Discharging capacitor

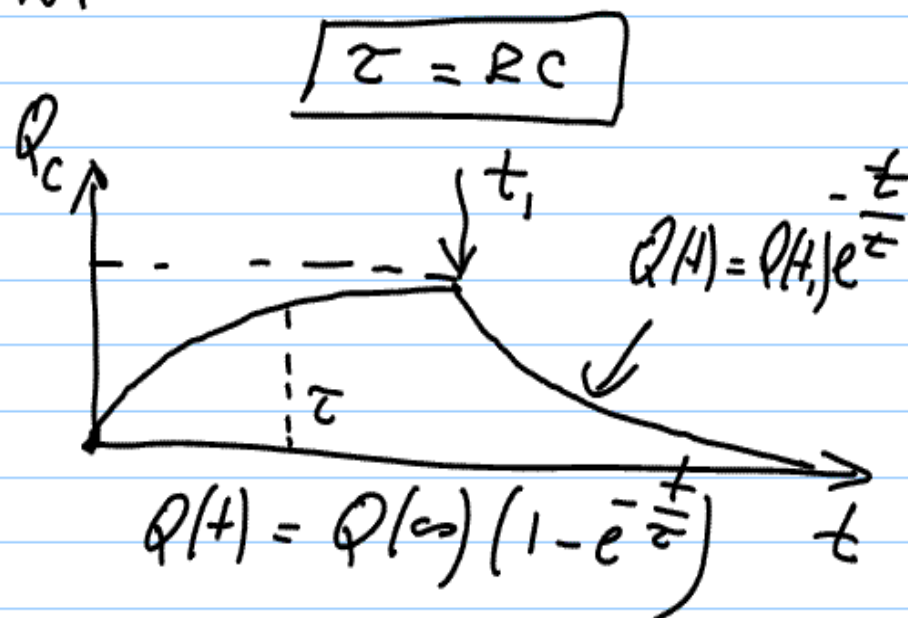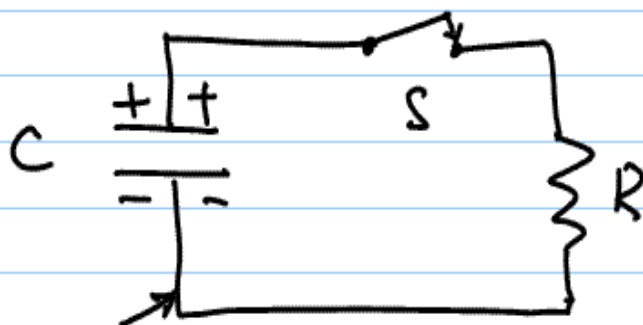

Kirchoff's rule:

Loop rule

$$\Delta V_C - IR = 0$$

$$I = \frac{dq}{dt}$$

$$I = -\frac{dQ}{dt}$$

q — charge through R

$$dq = -dQ$$

Q — charge on the capacitor

$$C = \frac{Q}{\Delta V_c} \Rightarrow \Delta V_c = \frac{Q}{C}$$

$$\frac{Q}{C} + \frac{dQ}{dt} R = 0$$

$$\frac{dt}{C} + \frac{dQ}{Q} R = 0.$$

$$\frac{dQ}{Q} R = - \frac{dt}{C}$$

$$\frac{dQ}{Q} = - \frac{1}{RC} dt$$

$$\int_{Q_0(0)}^{Q(t)} \frac{dQ}{Q} = - \frac{1}{RC} t \Big|_0^t$$

$$\ln|Q| \Big|_{Q_0}^{Q(t)} = - \frac{t}{RC} \Rightarrow \ln|Q(t)| - \ln|Q_0| = - \frac{t}{RC}$$


$$\ln \frac{Q(t)}{Q_0} = -\frac{t}{RC}$$

$$\boxed{\begin{matrix} \ln y \\ \ln y \\ e^{\ln y} = y \end{matrix}}$$


$$Q = Q_0 e^{-\frac{t}{RC}} \quad \tau = RC$$

$$Q(t) = Q_0 e^{-\frac{t}{\tau}} = Q_0 e^{-\frac{t}{\tau}}$$



(a)

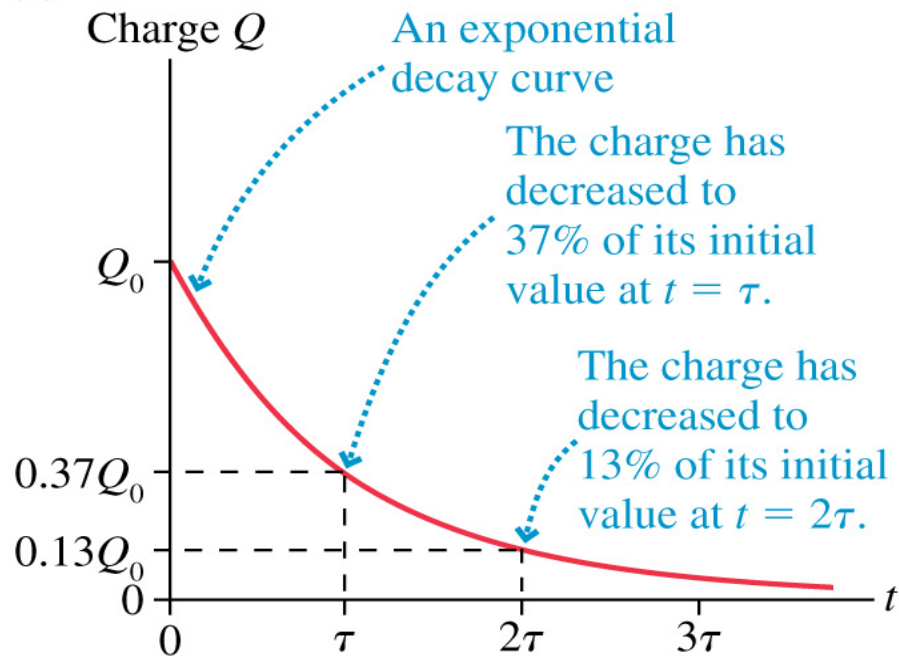

(b)

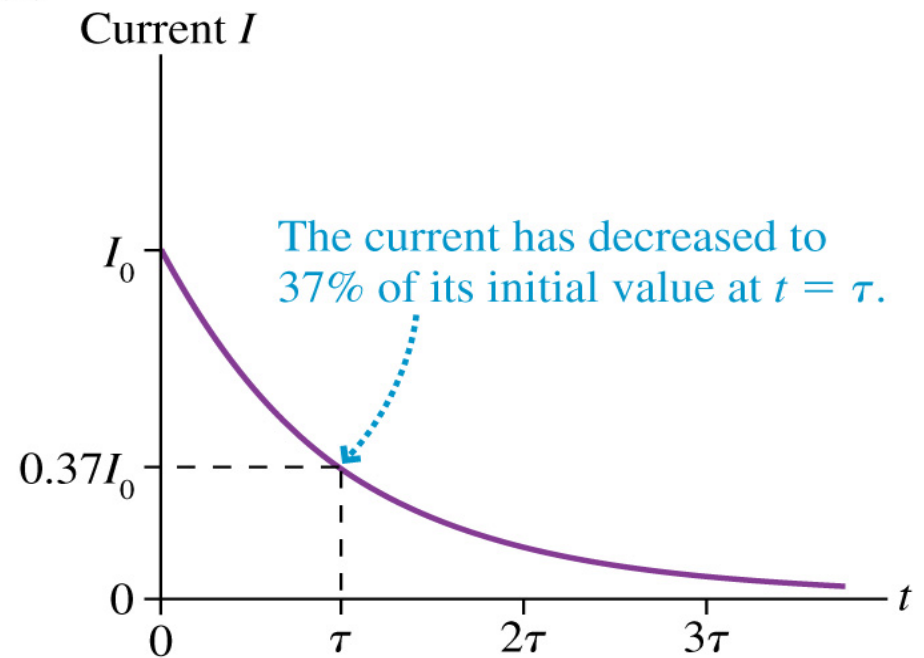

Charging Capacitor

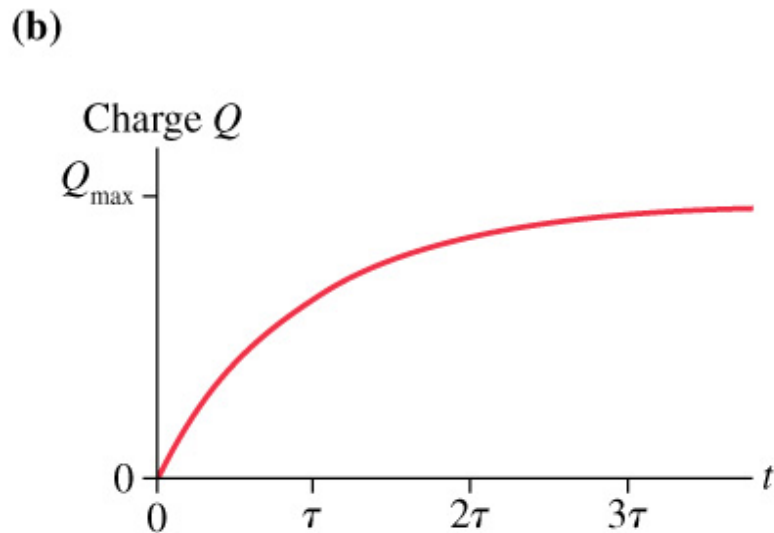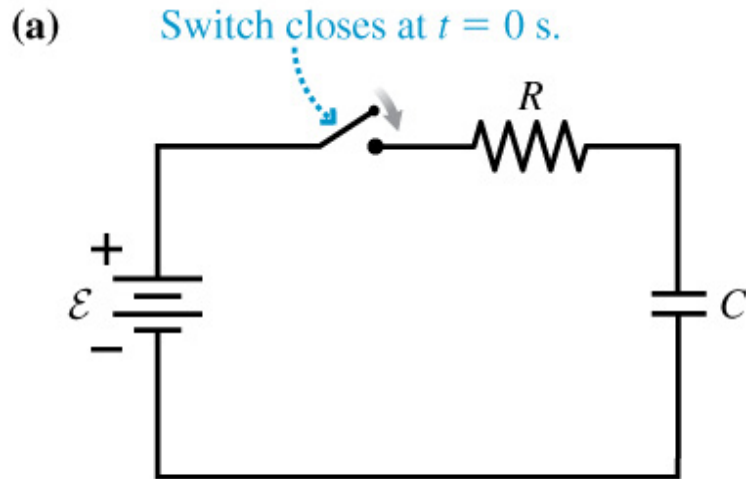

As a homework problem, you can show that the capacitor charge at time t is:


$$Q = Q_{\max}(1 - e^{-t/\tau})$$

A Couple of Problems from Chapter 31

Problem 57 Chapter 31

Note Title

3/17/2005

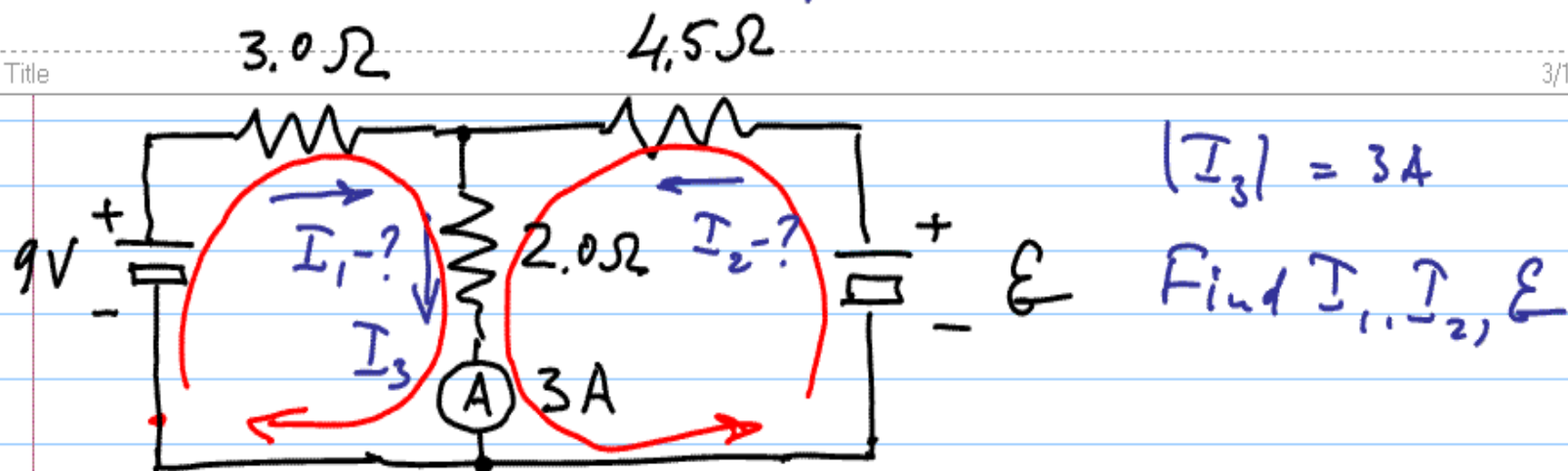

- Decide on direction of the currents
 - Decide about directions of loops
- Red color used for loops

$$+9V - I_1 \cdot 3 - 3 \cdot 2 = 0 \Rightarrow 3I_1 = 9 - 6 = 3 \Rightarrow \underline{I_1 = 1A}$$

$$+\mathcal{E} - I_2 \cdot 4.5 - 3 \cdot 2 = 0 \quad \begin{array}{l} \mathcal{E} - \text{not known} \\ I_2 - \text{not known} \end{array}$$


$$I_3 = I_1 + I_2 \Rightarrow I_2 = I_3 - I_1 = 3 - 1 = 2A$$

$$\mathcal{E} = 6 + I_2 \cdot 4.5 = 6 + 9 = 15V$$

Problem 56 Chapter 31

Note Title

3/21/2005

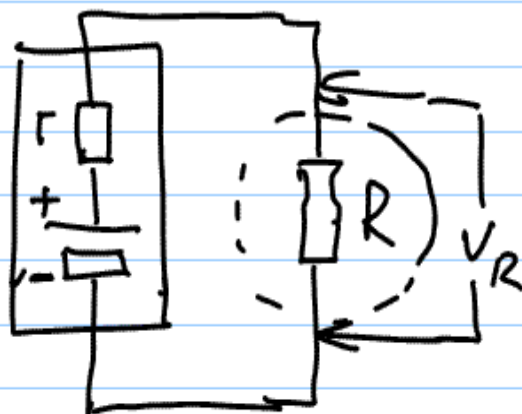

$$P_R = \underline{I} \cdot V_R = \underline{I}^2 \cdot R = \frac{V_R^2}{R}$$

$$V_R = \underline{I} \cdot R$$

$$\underline{I} = \frac{V_R}{R}$$

$$\underline{I} = \frac{\mathcal{E}}{r + R}$$

$$P_R = \frac{\mathcal{E}^2 \cdot R}{(r + R)^2} = \underbrace{(\mathcal{E}^2 \cdot R)}_u \underbrace{\frac{1}{(r + R)^2}}_v = u \cdot v$$

$$\frac{\partial P_R}{\partial R} = 0$$

$$P' = u' \cdot v + v' \cdot u$$

$$\frac{\partial P}{\partial R} = \frac{\partial u}{\partial R} \cdot v + \frac{\partial v}{\partial R} \cdot u$$



$$\begin{aligned}
 \frac{\partial P_R}{\partial R} &= \underbrace{\varepsilon^2 \frac{1}{(\Gamma + R^2)^2}}_{\frac{\partial u}{\partial R}} + \underbrace{\frac{(-2) \cdot \varepsilon^2 \cdot R}{(\Gamma + R)^3}}_{\frac{\partial v}{\partial R}} = \\
 &= \frac{\varepsilon^2 (\Gamma + R) - 2 \varepsilon^2 R}{(\Gamma + R)^3} = \frac{\varepsilon^2 [\Gamma + R - 2R]}{(\Gamma + R)^3} = \\
 &= \frac{\varepsilon^2 [\Gamma - R]}{(\Gamma + R)^3} = 0 \quad \boxed{\Gamma = R}
 \end{aligned}$$

End of Lecture 13
 Reading: Chapter 31
 Review for Quiz 6
 HW7