

Lecture 19: Chapter 33, November 8 2005

Energy in Inductor

$$P_{\text{elec}} = I \Delta V, \quad \Delta V_L = -L \frac{dI}{dt}$$

$$P_{\text{elec}} = I \Delta V_L = -L I \frac{dI}{dt}$$


$P_{\text{elec}} < 0$ since the current is losing energy

This energy is transferred to L :

$$\frac{du_L}{dt} = +L I \frac{dI}{dt}, \quad \text{assume } u_L = 0 \text{ at } I = 0$$

$$u_L = L \int_0^I I dI = \frac{1}{2} L I^2 \quad \begin{array}{l} \text{Compare to C:} \\ \downarrow \\ \longleftrightarrow u_C = \frac{1}{2} C (\Delta V)^2 \end{array}$$

LC Circuits

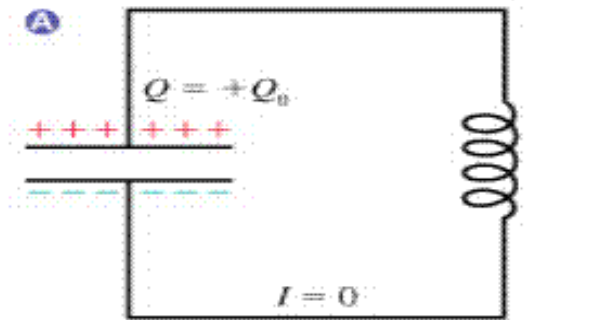


Maximum capacitor charge is like a fully stretched spring.

The current continues until the initial capacitor charge is restored.



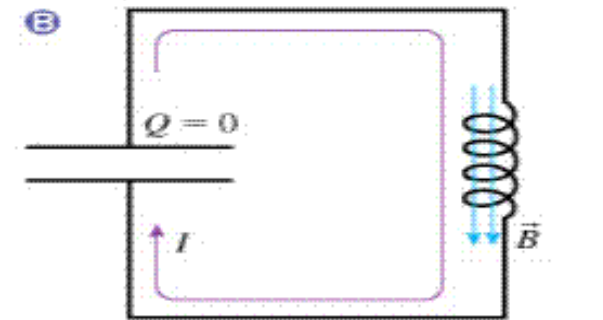
The capacitor discharges until the current is a maximum.




Maximum current is like the block having maximum speed.



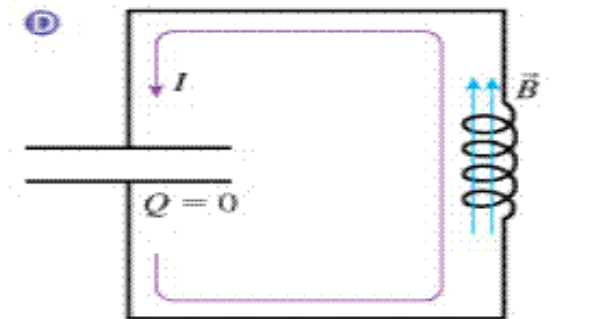
The current can't stop. It continues until the capacitor is fully recharged with the opposite polarization.



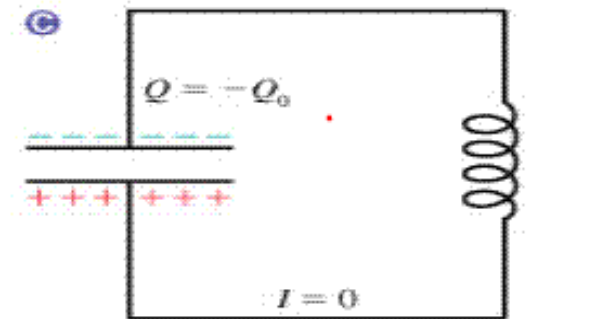Now the discharge goes in the opposite direction.



$\omega - ?$

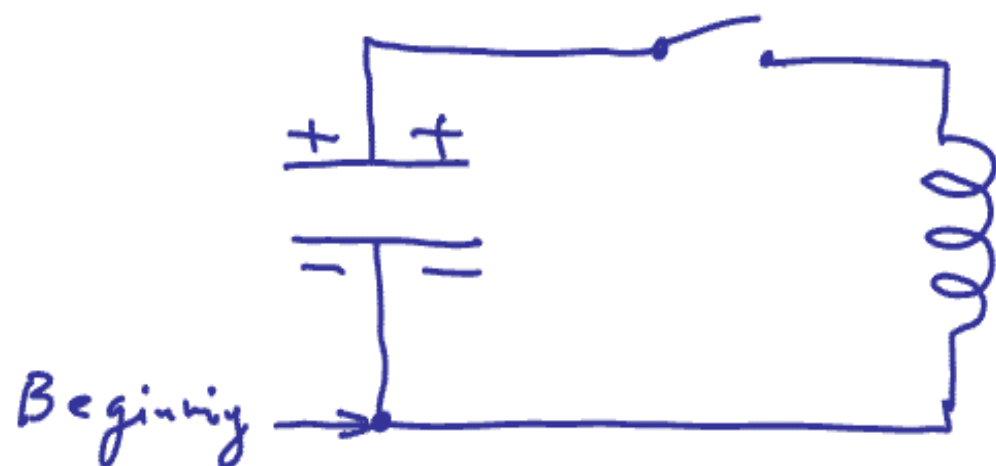

$$\Delta V_C + \Delta V_L = 0 -$$

Loop rule

$$\begin{cases} \Delta V_C = \frac{Q}{C} \\ \Delta V_L = -L \frac{dI}{dt} \end{cases}$$

$$\frac{Q}{C} - L \frac{dI}{dt} = 0,$$

but $I = \frac{dq}{dt}$

$$\boxed{\frac{Q}{C} + L \frac{d^2 Q}{dt^2} = 0}$$


$$\frac{d^2 Q}{dt^2} = -\frac{1}{LC} Q$$

q - current through the circuit


$$dq = -dQ$$

Q - current on the capacitor

Capacitor
charge Q

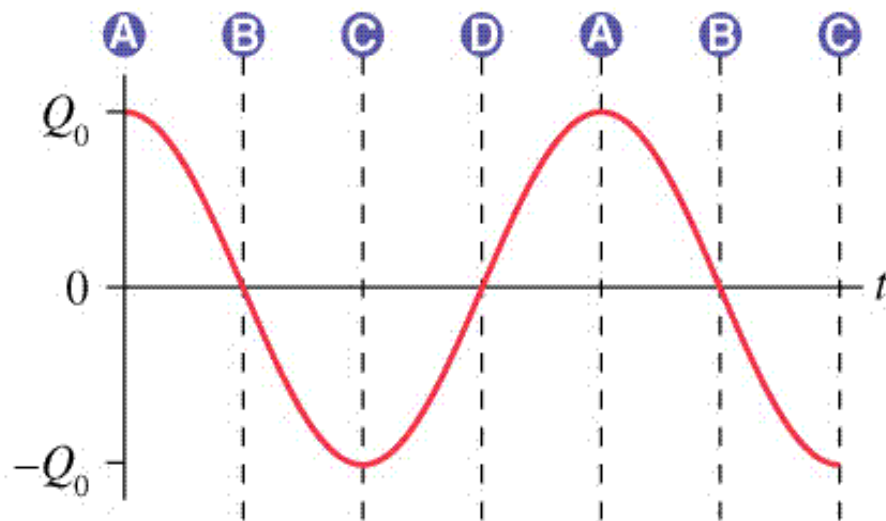

Inductor
current I

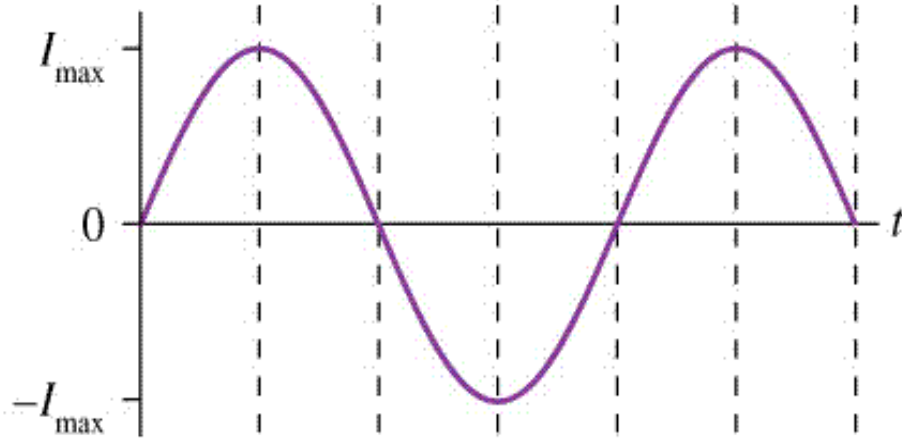

$$\frac{d^2 x}{dt^2} = -\frac{k}{m} x$$

$$\begin{cases} x \rightarrow Q \\ \frac{k}{m} \rightarrow \frac{1}{LC} \end{cases}$$

$$x = x_0 \cdot \cos \omega t$$

$$\omega = \sqrt{\frac{k}{m}}$$

$$Q(t) = Q_0 \cdot \cos \omega t$$


$$\omega = \sqrt{\frac{1}{LC}}$$

Check (substitute)

LR Circuits

(a)

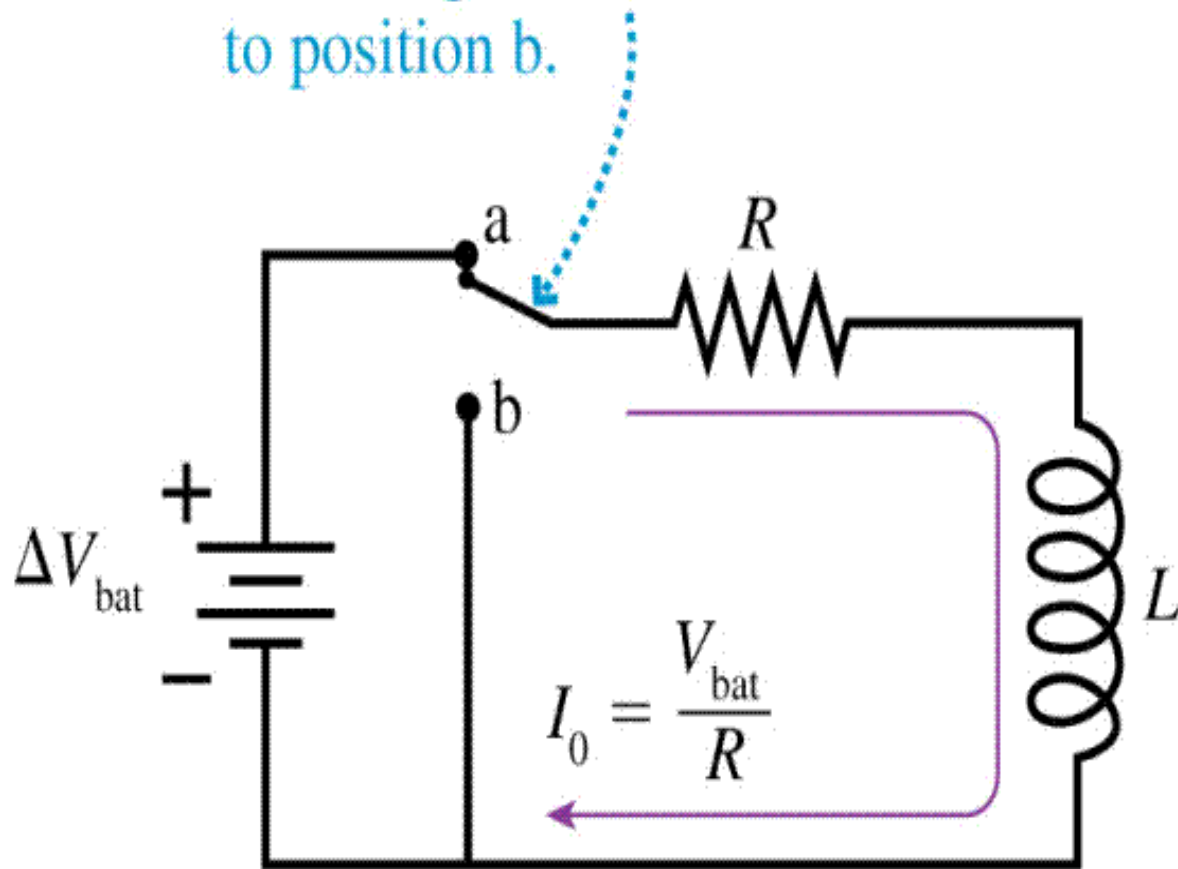The switch has been in this position for a long time. At $t = 0$ it is moved to position b.



$$\Delta V_L = -L \frac{d\bar{I}}{dt}$$

$$\Delta V_R + \Delta V_L = 0$$


Loop rule

$$\Delta V_R = -\bar{I}R$$
$$\Delta V_L = -L \frac{d\bar{I}}{dt}$$

$$-\bar{I}R - L \frac{d\bar{I}}{dt} = 0$$

$$\frac{d\bar{I}}{\bar{I}} = -\frac{R}{L} dt = -\frac{dt}{L/R}$$

(b)

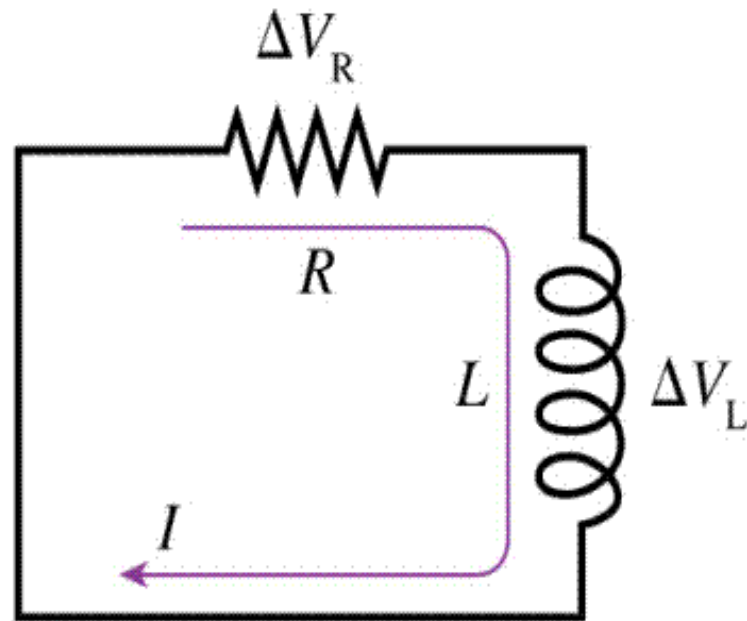

This is the circuit with the switch in position b. The inductor prevents the current from stopping instantly.

Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley

Start at $t=0 \rightarrow I_0$
Finish at $t \rightarrow I(t)$

$$\int_{I_0}^{I(t)} \frac{dI}{I} = -\frac{1}{(L/R)} \int_0^t dt$$

$$\ln I \Big|_{I_0}^{I(t)} = \ln I - \ln I_0$$

$$= \ln \frac{I}{I_0} = -\frac{t}{(L/R)}$$


$$\ln \frac{I}{I_0} = -\frac{t}{(L/R)}$$

$$e^{\ln \frac{I}{I_0}} = e^{-\frac{t}{(L/R)}}$$

$$\tau = \frac{L}{R}$$

$$\frac{I}{I_0} = e^{-\frac{t}{\tau}}$$

The Current Decay in LR Circuit

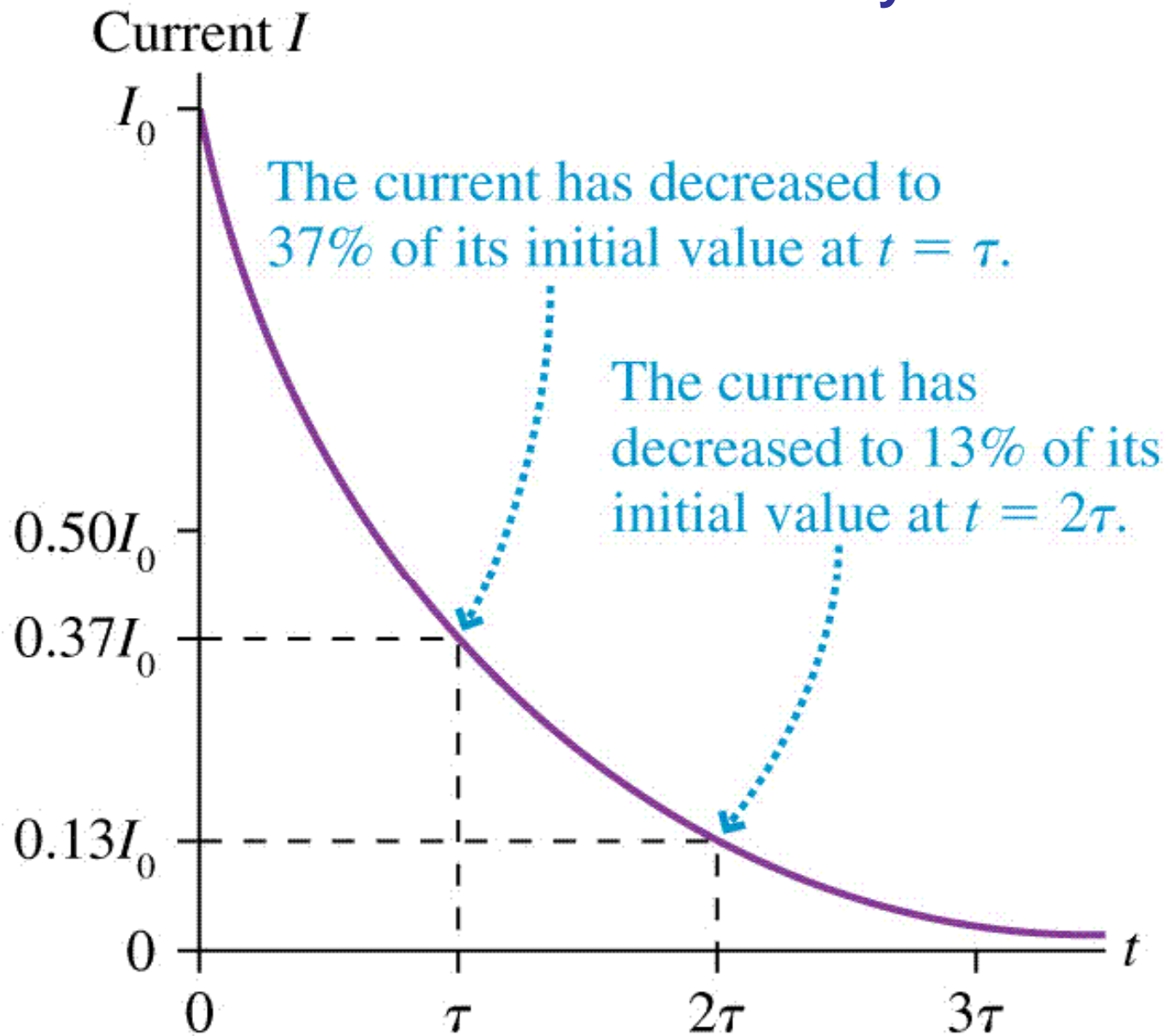

$$I(t) = I_0 e^{-\frac{t}{\tau}}$$
$$\tau = \frac{L}{R}$$

End of Lecture 19
Reading: Entire
Chapter 33
Review for Quiz 9
HW9