
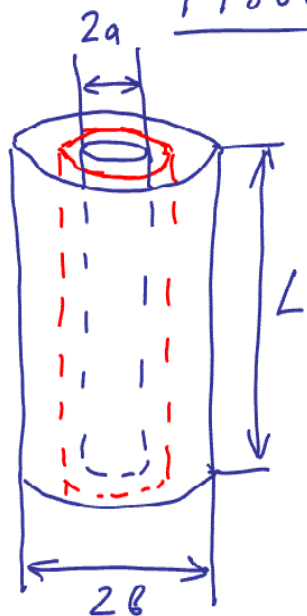


Problem 1

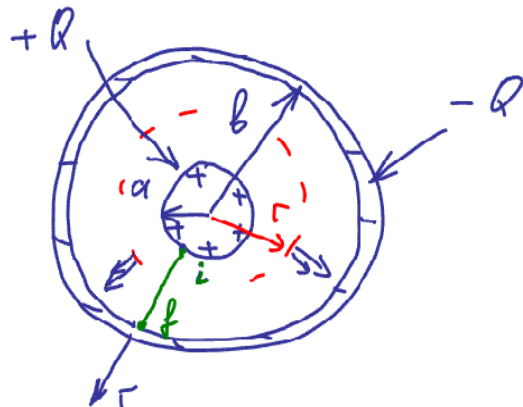

Derive an expression for the capacitance of the cylindrical capacitor in terms of a , b , L and ϵ_0 .



First step: Assume Q

Second step: Calculating $E(r)$ using Gauss's Law

$$\oint \vec{E} \cdot d\vec{A} = \frac{q_{enc}}{\epsilon_0} \leftarrow \text{Gauss's Law}$$

$$\vec{E} \parallel d\vec{A} \Rightarrow \vec{E} \cdot d\vec{A} = E \cdot dA$$

$$\oint E \cdot dA = E \oint dA = E \cdot 2\pi r \cdot L$$

$$q_{enc} = +Q$$

$$E \cdot 2\pi r \cdot L = \frac{Q}{\epsilon_0}$$

$$E(r) = \frac{1}{2\pi \epsilon_0} \frac{Q}{L \cdot r}$$

Third step: Finding $\Delta V = -\int_i^f \vec{E} \cdot d\vec{s}$



The path $i \rightarrow f$ is indicated on the sketch, it is selected to be along radial direction $\nabla \vec{E} \cdot d\vec{s}$, $E > 0$, $ds = dr > 0$

$$\vec{E} \parallel d\vec{s} \Rightarrow \vec{E} \cdot d\vec{s} = \underline{E(r) \cdot dr}$$

$$\Delta V = V_f - V_i < 0$$

$$|\Delta V| = |V_f - V_i| = + \int_i^f \vec{E} \cdot d\vec{s} = \int_i^f E(r) \cdot dr = \int_a^b E(r) \cdot dr = \int_a^b \frac{1}{2\pi \epsilon_0} \frac{Q}{L \cdot r} dr =$$

$$= \frac{Q}{2\pi \epsilon_0 \cdot L} \int_a^b \frac{dr}{r} = \frac{Q}{2\pi \epsilon_0 \cdot L} \ln r \Big|_a^b =$$


$$= \frac{Q}{2\pi \epsilon_0 \cdot L} (\ln b - \ln a) = \frac{Q}{2\pi \epsilon_0 \cdot L} \ln \frac{b}{a}$$

Last step: Calculate C using the definition of capacitance $C = \frac{Q}{\Delta V}$

$$C = \frac{Q}{\frac{Q}{2\pi \epsilon_0 \cdot L} \ln \frac{b}{a}} = \frac{2\pi \epsilon_0 \cdot L}{\ln \frac{b}{a}}$$


Problem 2

Sample 31-63

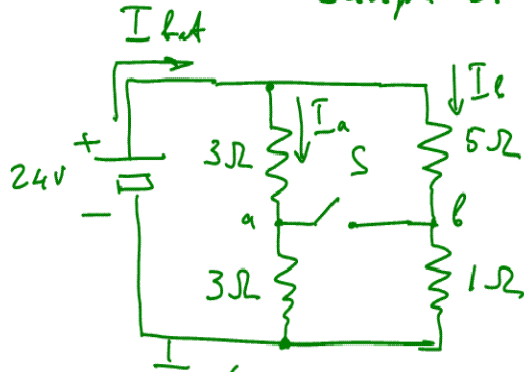

What is I_{tot} and V_{ab} when the switch is:
a) Open-?
b) Closed-?

(a) - Open S

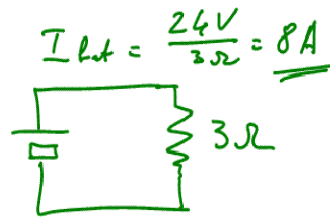

Branch a: $24V = I_a(3\Omega + 3\Omega) \Rightarrow I_a = \frac{24V}{6\Omega} = 4A$

Branch b: $24V = I_b(5\Omega + 1\Omega) \Rightarrow I_b = \frac{24V}{6\Omega} = 4A$

$V_a = \underbrace{V_{initial}}_0 + I_a \cdot (3\Omega) = 4A \cdot 3\Omega = 12V$

$V_b = 0 + I_b \cdot (1\Omega) = 4A \cdot 1\Omega = 4V$

$V_{ab} = V_a - V_b = 12V - 4V = 8V$

Let us start alternatively from the

top part of the circuit: (V_{top})

$V_a = V_{top} - I_a \cdot (3\Omega) = V_{top} - 12V$

$V_b = V_{top} - I_b \cdot (5\Omega) = V_{top} - 20V$

$V_{ab} = V_a - V_b = \cancel{V_{top}} - 12V - \cancel{V_{top}} + 20V = 8V$
So, it does not matter where we start, the result is the same!

(b) - S-closed



$\frac{1}{R_{35}} = \frac{1}{3} + \frac{1}{5} = \frac{5+3}{15} = \frac{8}{15}$
 $R_{35} = \frac{15}{8}\Omega$

$\frac{1}{R_{31}} = \frac{1}{3} + \frac{1}{1} = \frac{1+3}{3} = \frac{4}{3}$
 $R_{31} = \frac{3}{4}\Omega$



$R_{ref} = R_{35} + R_{31} = \frac{15}{8} + \frac{3}{4} = \frac{15+6}{8} = \frac{21}{8}\Omega$

$I_{tot} = \frac{24V}{\frac{21}{8}\Omega} = 9.143A$

$V_{ab} = 0$

Problem 3

A couple of problems 30-45 and 29-48

Problem 30-45


Given $V = (150x^2 - 200y^2) [V]$,

where x and y - in meters

What is the strength and direction of the el. field at point $(x = 2.0 \text{ m}, y = 2.0 \text{ m})$?

$$E_x = -\frac{\partial V}{\partial x} = -2x \cdot 150 = -300x = -600 \frac{V}{m}$$
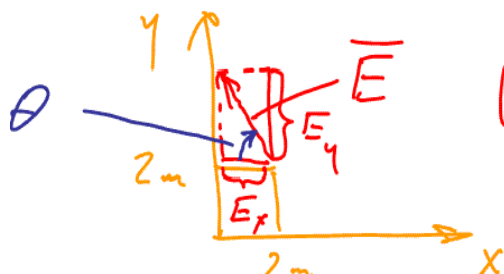
$$E_y = -\frac{\partial V}{\partial y} = +2y \cdot 200 = 400y = 800 \frac{V}{m}$$




$$|\vec{E}| = \sqrt{E_x^2 + E_y^2} = \sqrt{(-600)^2 + (800)^2} = 1000 \frac{V}{m}$$

$$\tan \theta = \frac{E_y}{|E_x|} = \frac{800}{600} = \frac{4}{3} \Rightarrow \theta = 53.1^\circ$$

above the
-x-axis

Problem 29-48

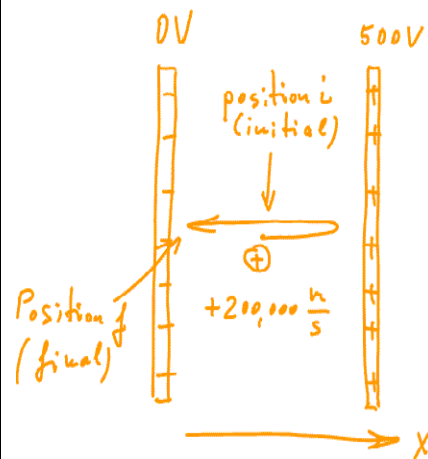

A proton is fired with $v = 2.0 \times 10^5 \frac{m}{s}$ from the mid point of a capacitor towards the + plate.

a) Show that v is insufficient to reach + plate

b) What is the proton velocity (v_f) as it collides with the negative plate?

(a) Inside the capacitor $V(x) = E \cdot x \Rightarrow V_i = \frac{500V - 0V}{2} = 250V$

The energy required to reach + plate:

$$\Delta U = e\Delta V = 1.6 \times 10^{-19} C \cdot (250V) = 4 \times 10^{-17} J$$

The proton kinetic energy is:

$$K = \frac{1}{2} m v_i^2 = \frac{1}{2} (1.67 \times 10^{-27} kg) \cdot (2.0 \times 10^5 \frac{m}{s})^2 = 3.34 \times 10^{-17} J$$

$K < \Delta U \Rightarrow$ not enough energy to reach + plate

(b) Use energy conservation:

$$E_i = E_f$$

$$K_i + U_i = K_f + U_f$$

$$\frac{1}{2} m v_i^2 + qV_i = \frac{1}{2} m v_f^2 + qV_f \Rightarrow$$

$$\frac{1}{2} m v_f^2 = \frac{1}{2} m v_i^2 + q(V_i - V_f)$$


$$v_f = \sqrt{v_i^2 + \frac{2q}{m} (V_i - V_f)} = \sqrt{(2 \times 10^5 \frac{m}{s})^2 + \frac{2(1.6 \times 10^{-19} C)(250V - 0V)}{1.67 \times 10^{-27} kg}}$$

$$= 2.96 \times 10^5 \frac{m}{s}$$

Problem 4

Samples 31-77 and 30-31


Problem 31-77

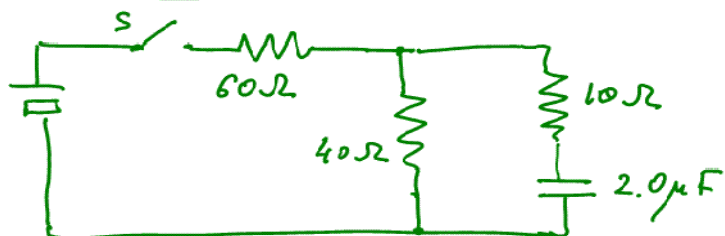

The switch S has been closed for a very long time

- What is the charge on the capacitor?
- The switch is open at $t = 0$ s. At what time has the charge on the capacitor decreased to 10% of its initial value?

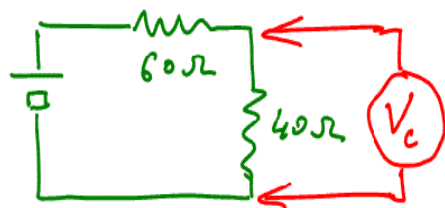- (a) In steady state the capacitor is a break $\Rightarrow$
An equivalent circuit is a voltage divider!



Voltage available for the capacitor:


$$V_{40} = \frac{\mathcal{E} \cdot 40}{60 + 40} = 40V$$

In steady state I through 10Ω resistor $= 0 \Rightarrow$

$$V_{10} = I_{10} \cdot 10 = 0 \Rightarrow V_C = V_{40} = 40V$$

$$\text{Since } C = \frac{Q}{V_C} \Rightarrow Q = C \cdot V_C = (2 \times 10^{-6} F) \cdot (40V) = \underline{\underline{80\mu C}}$$

Reopening creates a new circuit:

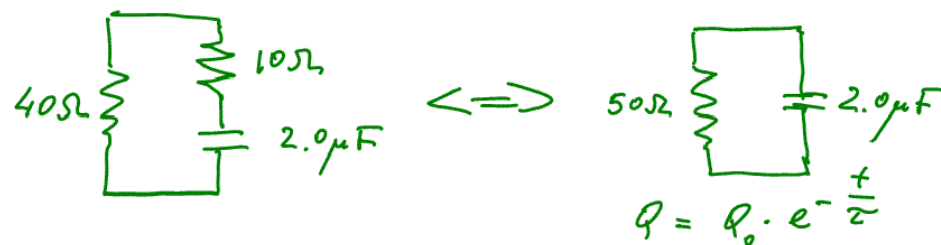

$$Q_0 = 80\mu C$$

$$\tau = RC = 50\Omega \cdot 2.0 \times 10^{-6} F = \underline{\underline{10^{-4} s}}$$

$$Q(t) = 0.1 \cdot Q_0 \Rightarrow$$

$$0.1 Q_0 = Q_0 \cdot e^{-\frac{t}{\tau}}$$

$$\ln 0.1 = \ln(e^{-\frac{t}{\tau}}) = -\frac{t}{\tau}$$

$$-2.3 = -\frac{t}{\tau} \Rightarrow t = 2.3 \cdot \tau = 2.3 \cdot 10^{-4} s = \underline{\underline{0.23ms}}$$

Problem 30-31


Capacitor 2 has half the capacitance and twice the potential difference as capacitor 1

$$(C_2 = \frac{1}{2} C_1, \Delta V_{C_2} = 2 \Delta V_{C_1})$$

What is the ratio of their potential energies $\frac{U_{C_1}}{U_{C_2}}$?

$$\frac{U_{C_1}}{U_{C_2}} = \frac{\frac{1}{2} C_1 (\Delta V_{C_1})^2}{\frac{1}{2} C_2 (\Delta V_{C_2})^2} = \frac{C_1 (\Delta V_{C_1})^2}{(\frac{1}{2} C_1) \cdot 4 (\Delta V_{C_1})^2} = \frac{1}{2}$$

Problem 5

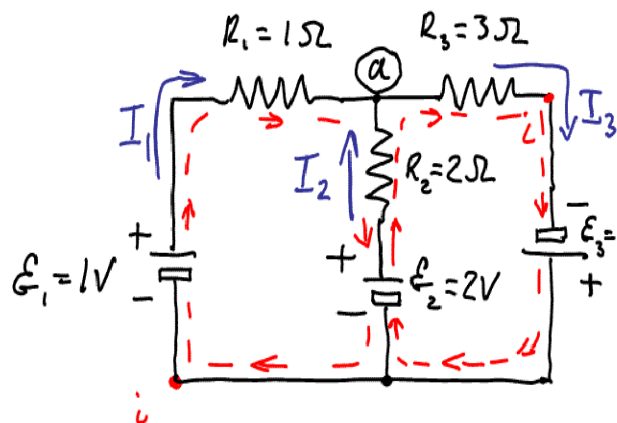

Find the currents I_1 , I_2 and I_3 in each resistor using Kirchhoff's Law

Step 1: Assume directions for the currents

I_1 , I_2 and I_3 in all branches.

If your assumption is correct you will eventually find this current I_i with sign +

If you made a wrong assumption, you will find sign -. In any case you are safe to assume directions for the currents **ARBITRARY**.

Step 2: Assume directions (clockwise or counterclockwise) of making loops.

Generally, the directions are selected **ARBITRARY**

In this example we selected clockwise directions for both small loops starting from the point indicated "a"

Step 3: To find three unknowns I_1 , I_2 and I_3 we need three independent equations.

Let us use two loop rules and one junction rule. They will give us a complete system of independent equations.

Left loop:

$$1 - I_1 \cdot 1 + I_2 \cdot 2 - 2 = 0 \quad (1)$$

we go through the resistor R_1 with the current. Hence, according to the "resistor" rule the sign is negative

we go through R_2 against the current $I_2 \Rightarrow$ the sign is positive

Right loop:

$$3 + 2 - I_2 \cdot 2 - I_3 \cdot 3 = 0 \quad (2)$$

Junction rule at point a:

$$I_1 + I_2 = I_3 \quad (3)$$

substitute (3) in (2):

$$5 - I_2 \cdot 2 - (I_1 + I_2) \cdot 3 = 0$$

$$5 - I_2 \cdot 5 - I_1 \cdot 3 = 0$$

$$\text{From (1): } I_1 = -1 + I_2 \cdot 2$$

plug it into the previous eq.:

$$5 - I_2 \cdot 5 - (-1 + I_2 \cdot 2) \cdot 3 = 0$$

$$5 - I_2 \cdot 5 + 3 - 6 I_2 = 0$$

$$8 = 11 \cdot I_2 \Rightarrow I_2 = \frac{8}{11} \text{ A}$$

$$I_1 = -1 + 2 I_2 = -1 + \frac{16}{11} = \frac{-11 + 16}{11} = \frac{5}{11} \text{ A}$$

$$I_3 = I_1 + I_2 = \frac{8}{11} + \frac{5}{11} = \frac{8 + 5}{11} = \frac{13}{11} \text{ A}$$