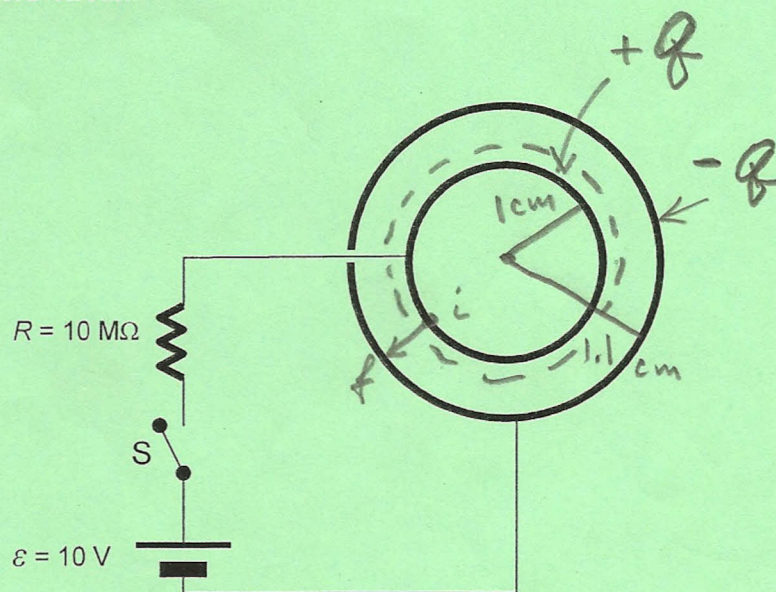


1. Figure shows a spherical capacitor. The inner sphere has a radius $a = 1$ cm and the outer sphere has a radius $b = 1.1$ cm. Assume that a maximum charge of q Coulombs can accumulate on the plates of capacitor when switch S has been closed for a long time, determine.

- Using Gauss's law, derive an expression for the electric field inside the capacitor.
- Determine an expression for the potential difference across the capacitor in terms of a , b , q and $K = 1/(4\pi\epsilon_0)$.
- Derive an expression for the capacitance of the spherical capacitor in terms of a , b , q and $K = 1/(4\pi\epsilon_0)$.
- Determine the time constant of the RC circuit.



$$a) \oint_C \vec{E} \cdot d\vec{A} = \frac{q_{enc}}{\epsilon_0}$$

$$|\vec{E}||d\vec{A}| \Rightarrow \vec{E} \cdot d\vec{A} = |\vec{E}| \cdot |d\vec{A}| \cdot \cos 0^\circ = E \cdot dA$$

$$\oint_C \vec{E} \cdot d\vec{A} = \int_C E \cdot dA = E(r) \cdot \int_C dA = E(r) \cdot 4\pi r^2, \quad q_{enc} = +q$$

$$E(r) \cdot 4\pi r^2 = \frac{q}{\epsilon_0} \Rightarrow E(r) = \frac{1}{4\pi\epsilon_0} \cdot \frac{q}{r^2}$$

$$b) V_f - V_i = - \int_i^f \vec{E} \cdot d\vec{s}$$

$$\Delta V = V_i - V_f = \int_i^f \vec{E} \cdot d\vec{s} = \int_a^b \frac{1}{4\pi\epsilon_0} \cdot \frac{q}{r^2} dr = \frac{q}{4\pi\epsilon_0} \int_a^b \frac{dr}{r^2} =$$

$$= \frac{q}{4\pi\epsilon_0} \left(-\frac{1}{r} \right) \Big|_a^b = \frac{q}{4\pi\epsilon_0} \left(\frac{1}{a} - \frac{1}{b} \right) = \frac{q}{4\pi\epsilon_0} \frac{b-a}{ab}$$

$$c) C = \frac{q}{\Delta V} = \frac{\cancel{q} \cdot 4\pi\epsilon_0 \cdot ab}{\cancel{q}(b-a)} = 4\pi\epsilon_0 \frac{ab}{b-a} \quad (1)$$



$$d) \tau = RC = 4\pi\epsilon_0 \frac{abR}{b-a} =$$

$$= \left(\frac{1}{4\pi\epsilon_0} \right)^{-1} \times \frac{10^{-2} \cdot 1.1 \times 10^{-2} \cdot 10^{-7}}{0.1 \cdot 10^{-2}} = \left(9 \times 10^9 \right)^{-1} \frac{1.1 \cdot 10^5}{0.1} =$$

$$= 0.11 \times 10^{-9} \times 11 \times 10^5 = 1.2 \times 10^{-4} \text{ s} = \underline{\underline{0.12 \text{ ms}}}$$

2. In the circuit shown, $R_1 = 3 \Omega$, $R_2 = 6 \Omega$, $R_3 = 4 \Omega$, $C_1 = 2 \mu\text{F}$, $C_2 = 3 \mu\text{F}$, $C_3 = 4 \mu\text{F}$ and $\mathcal{E} = 12 \text{ V}$. Determine amount of charge accumulated on each capacitor, C_1 , C_2 and C_3 , after the switch S has been (a) open for a long time, and (b) closed for a long time.

(b) Switch closed for a long time

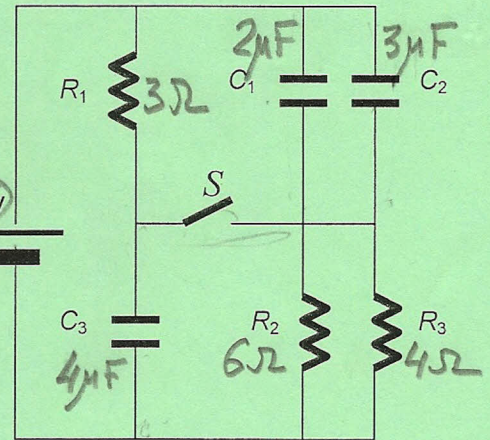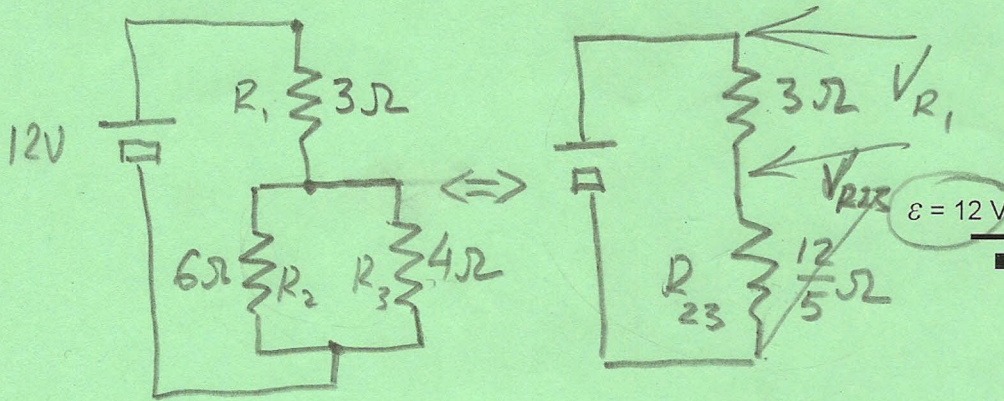

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{6} + \frac{1}{4} = \frac{2+3}{12} = \frac{5}{12}$$

$$R_{23} = \frac{12}{5} \Omega$$

$$V_{R_1} = \mathcal{E} \cdot \frac{R_3}{R_3 + R_{23}} = \frac{12 \cdot 3}{3 + \frac{12}{5}} = \frac{36}{\frac{15+12}{5}} = \frac{180}{27} = 6.666 \text{ V}$$

$$V_{R_{23}} = \mathcal{E} \cdot \frac{R_{23}}{R_3 + R_{23}} = \frac{12 \cdot \frac{12}{5}}{\frac{27}{5}} = \frac{144}{27} = 5.333 \text{ V}$$

$$C = \frac{Q}{V} \Rightarrow Q = C \cdot V$$


$$Q_{C_1} = C_1 \times V_{R_1} = 2 \mu\text{F} \cdot 6.666 \text{ V} = 13.33 \mu\text{C}$$

$$Q_{C_2} = C_2 \times V_{R_1} = 3 \mu\text{F} \cdot 6.666 \text{ V} = 20.0 \mu\text{C}$$

$$Q_{C_3} = C_3 \times V_{R_{23}} = 4 \mu\text{F} \cdot 5.333 \text{ V} = 21.33 \mu\text{C}$$

a) Switch open for long time

(4)

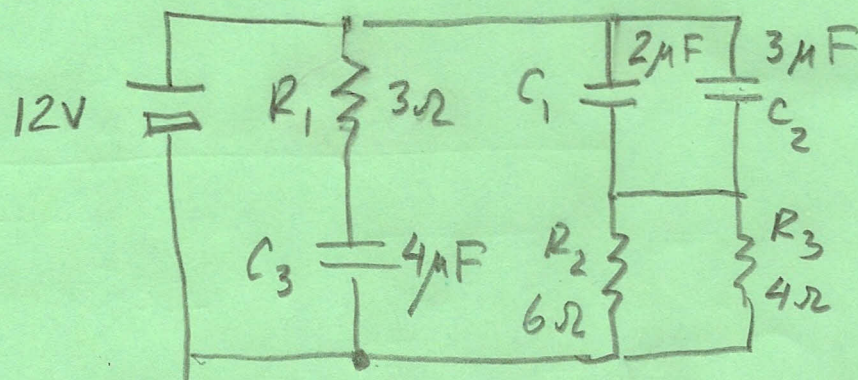


$$C_{12} = C_1 + C_2 = 2 + 3 = 5 \mu\text{F}$$

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} =$$

$$= \frac{1}{6} + \frac{1}{4} = \frac{2+3}{12} = \frac{5}{12}$$

$$R_{23} = \frac{12}{5} \Omega$$

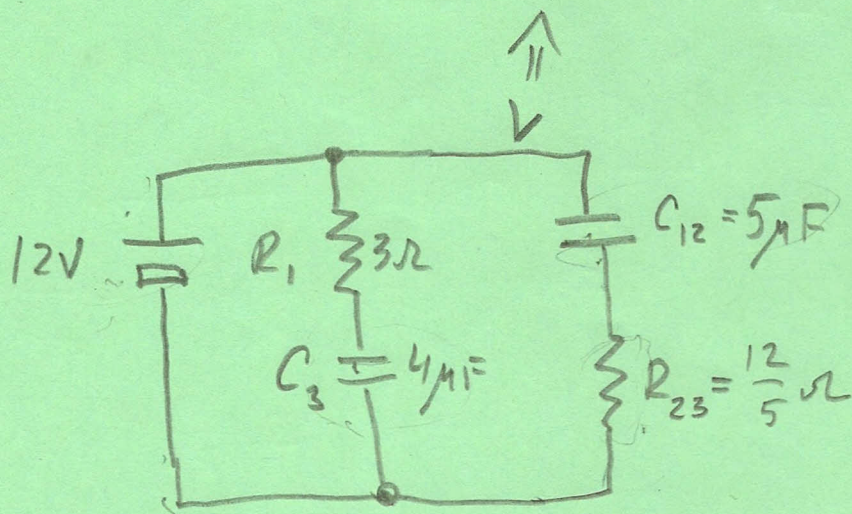


$$V_{C_3} = 12V, \quad Q_{C_3} = C_3 \cdot V_{C_3} = 4 \mu\text{F} \cdot 12V = \underline{\underline{48 \mu\text{C}}}$$

$$V_{C_{12}} = 12V, \quad Q_{C_1} = C_1 \cdot V_{C_{12}} = 2 \mu\text{F} \cdot 12V = \underline{\underline{24 \mu\text{C}}}$$

$$Q_{C_2} = C_2 \cdot V_{C_{12}} = 3 \mu\text{F} \cdot 12V = \underline{\underline{36 \mu\text{C}}}$$

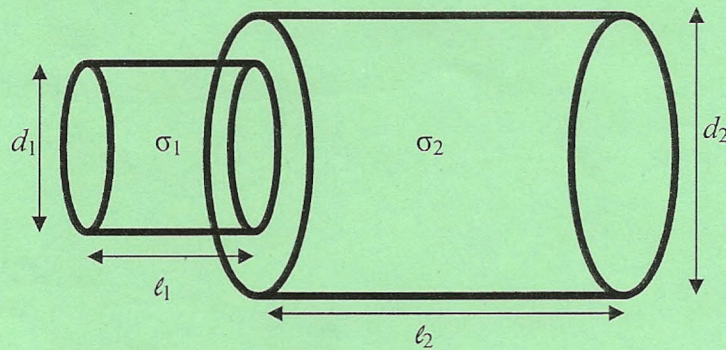3. A wire is made of two different metal segments with conductivities σ_1 and σ_2 respectively, as shown in Figure below. The two segments have different diameters and different lengths. When the wire is connected to a battery, the potential drop across each segment is the same. What is the ratio of σ_1 / σ_2 expressed in terms of ℓ_1 , ℓ_2 , d_1 , and d_2 where ℓ and d stand for length and diameter of wire segments respectively?



$$j = \frac{I}{A} = \sigma E, \quad V = E \cdot \ell, \quad E = \frac{I}{A \cdot \sigma}$$

$$I_1 = I_2 \quad (2)$$


$$V_1 = V_2 \Rightarrow E_1 \cdot \ell_1 = E_2 \cdot \ell_2$$

$$\frac{I_1 \cdot \ell_1}{A_1 \cdot \sigma_1} = \frac{I_2 \cdot \ell_2}{A_2 \cdot \sigma_2} \quad (5)$$

$$\frac{\sigma_1}{\sigma_2} = \frac{\ell_1 \cdot A_2}{A_1 \cdot \ell_2} = \left(\frac{\ell_1}{\ell_2} \right) \times \left(\frac{A_2}{A_1} \right) = \frac{\ell_1}{\ell_2} \left(\frac{\pi d_2^2}{\pi d_1^2} \right) = \frac{\ell_1}{\ell_2} \left(\frac{d_2}{d_1} \right)^2 \quad (3)$$

4. In the circuit shown, $R_1 = R_2 = R_3 = 10\ \Omega$, and $\mathcal{E}_1 = \mathcal{E}_2 = 10\text{ V}$. Using Kirchhoff's loop and junction laws, determine the currents I_1 , I_2 and I_3 flowing through R_1 , R_2 and R_3 respectively, where the direction of each current is as indicated in the figure below.

Properly written equations give (7)

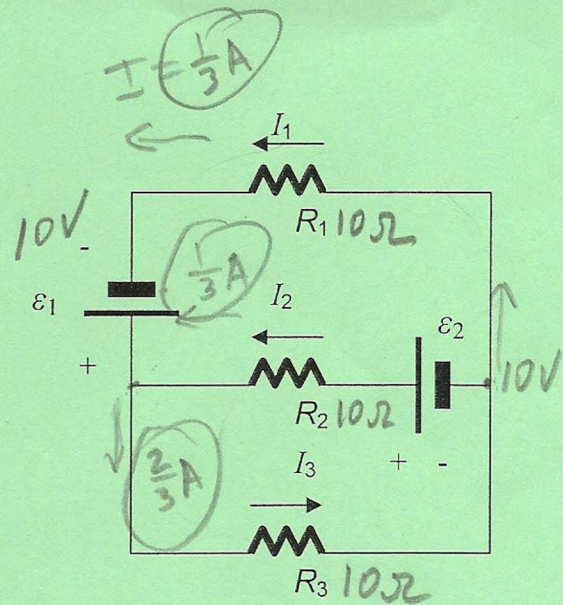

$$\begin{cases} -I_1 \cdot 10 + 10 + I_2 \cdot 10 - 10 = 0 & (1) \Rightarrow I_1 = I_2 \\ -I_3 \cdot 10 + 10 - I_2 \cdot 10 = 0 & (2) \Rightarrow 10I_2 = 10 - 10I_3 \\ I_1 + I_2 = I_3 & (3) \end{cases}$$

$I_2 = 1 - I_3$

~~$$I_2 = 10I_1 + 10$$~~

$$I_2 + I_2 = I_3, \quad 2I_2 = I_3$$


$$2(1 - I_3) = I_3$$

$$2 - 2I_3 = I_3$$

$$2 = 3I_3 \Rightarrow I_3 = \left(\frac{2}{3}\text{A}\right)$$

$$I_2 = 1 - \frac{2}{3} = \left(\frac{1}{3}\text{A}\right), \quad I_1 = \left(\frac{1}{3}\text{A}\right)$$

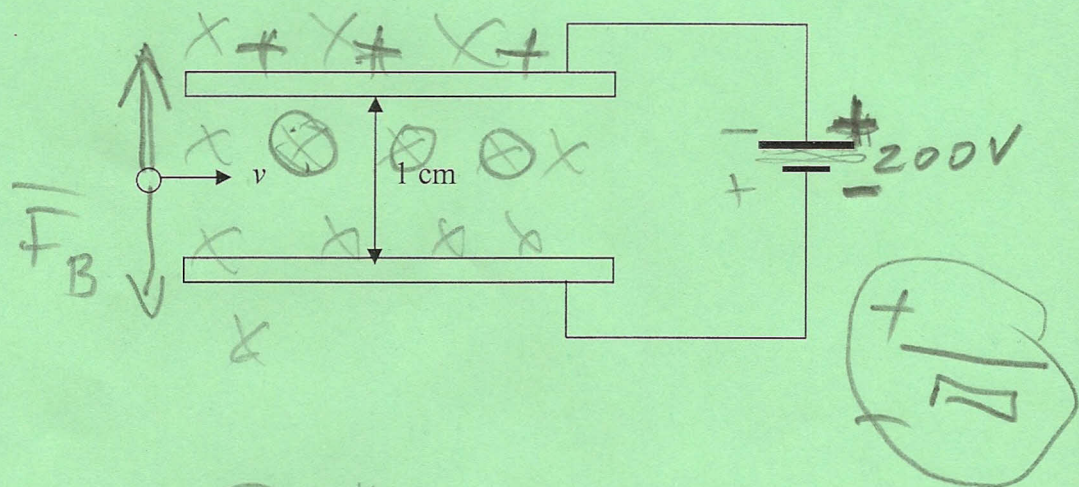5. An electron travels with speed 1.0×10^7 m/s between the two parallel charged plates shown in Figure below. The plates are separated by 1.0 cm and are charged by a 200 V battery. What magnetic field strength and direction will allow the electron to pass between the plates without being deflected?



$$v = 1.0 \times 10^7 \frac{\text{m}}{\text{s}}$$

If B is in page $(\otimes)$ then F_B is down $\downarrow$
 In this case $+$ of the battery should be connected to the top electrode to compensate: $\vec{F}_E + \vec{F}_B = 0.$ 5

$$|\vec{F}_E| = eE = e \cdot \frac{V}{d}$$


$$|\vec{F}_B| = |e\vec{v} \times \vec{B}| = e v B.$$

$$e \frac{V}{d} = e v B \Rightarrow B = \frac{V}{d \cdot v} = \frac{200}{10^{-2} \cdot 10^7}$$

$$= \frac{2 \cdot 10^2}{10^{-2} \cdot 10^7} = \frac{2 \cdot 10^4}{10^7} = 2 \cdot 10^{-3} \text{ (T)}.$$

However the second way is also possible if B is out of page $(\odot)$. In this case the top electrode is negative.

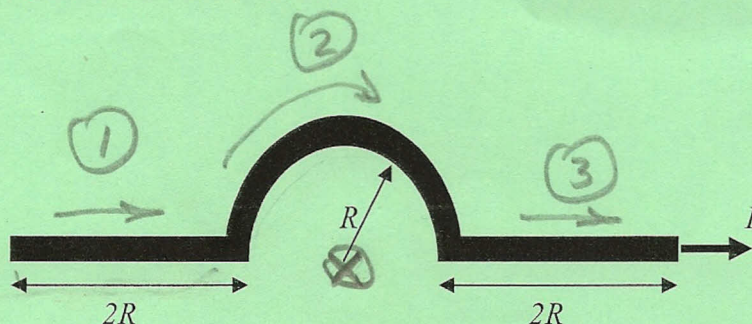6. Current I flows in the wire shown in Figure below. Use the Biot-Savart law to find an expression for the magnetic field strength at the center of the semicircle. What is the direction of the magnetic field at this point?



$$d\vec{B} = \frac{\mu_0}{4\pi} \frac{I d\vec{s} \times \hat{r}}{r^2}$$

For regions ① and ③

$d\vec{s} \parallel d\hat{r}$ or antiparallel. In any case
 $d\vec{s} \times \hat{r} = |d\vec{s}| \cdot |\hat{r}| \cdot \sin 0^\circ = 0 \Rightarrow$

$$dB_1 = dB_3 = 0 \Rightarrow$$

Total magnetic field from ① and ③ is zero.

For region ②:

$$d\vec{s} \perp d\hat{r} \Rightarrow d\vec{s} \times \hat{r} = |d\vec{s}| \times |\hat{r}| \times \sin 90^\circ = ds$$

$$dB_2 = \frac{\mu_0}{4\pi} \frac{I ds}{r^2} = \frac{\mu_0}{4\pi} \frac{IR}{R^2} \cdot d\theta = \frac{\mu_0 I}{4\pi R} d\theta$$

$$|ds| = R \cdot d\theta$$

$$B_2 = \int dB_2 = \int \frac{\mu_0 I}{4\pi R} \cdot d\theta =$$

$$= \frac{\mu_0 I}{4\pi R} \int_0^\pi d\theta = \frac{\mu_0 I}{4\pi R} \pi = \frac{\mu_0 I}{4R}$$